

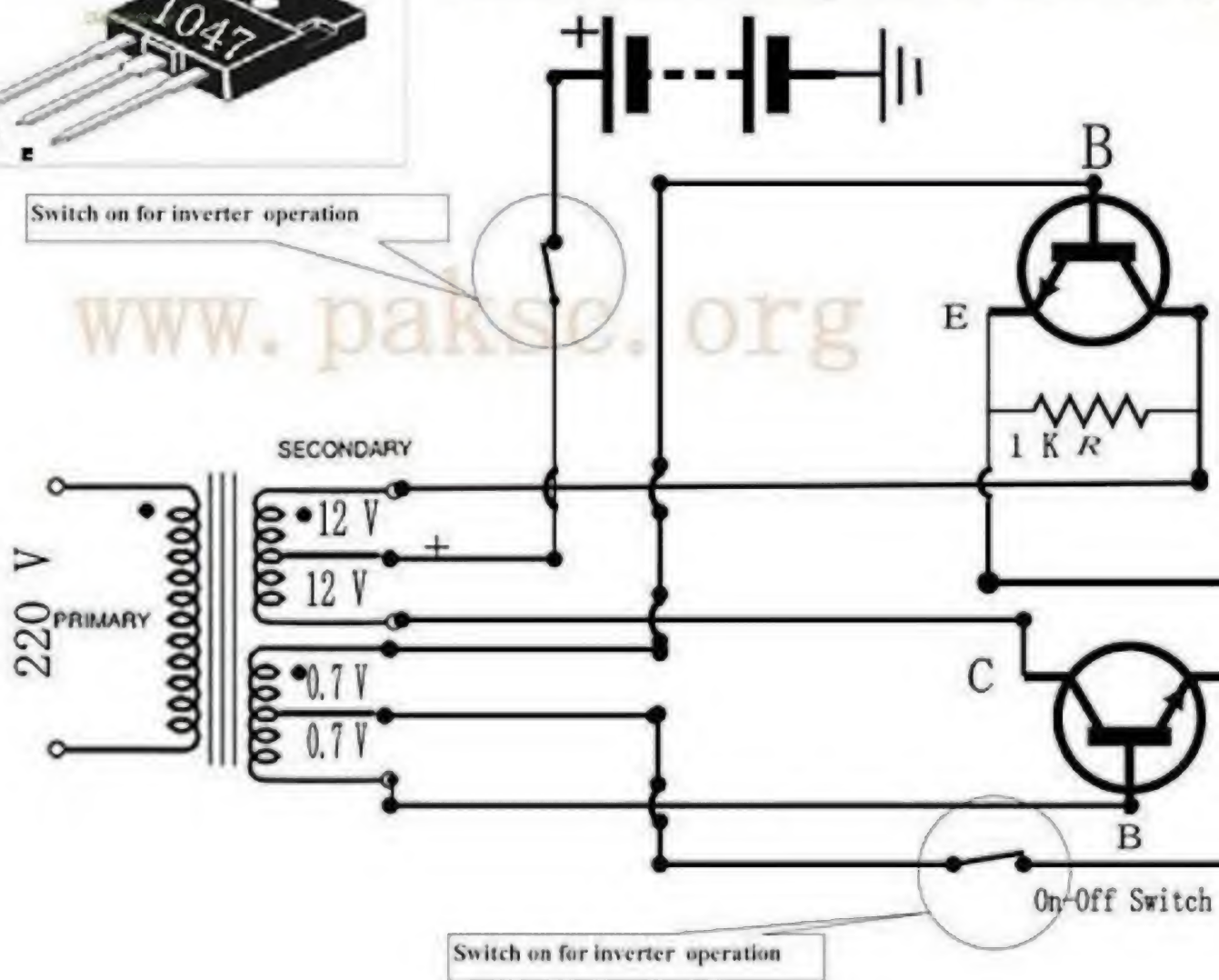


Switch on for inverter operation

inverter circuit diagram for inverter op

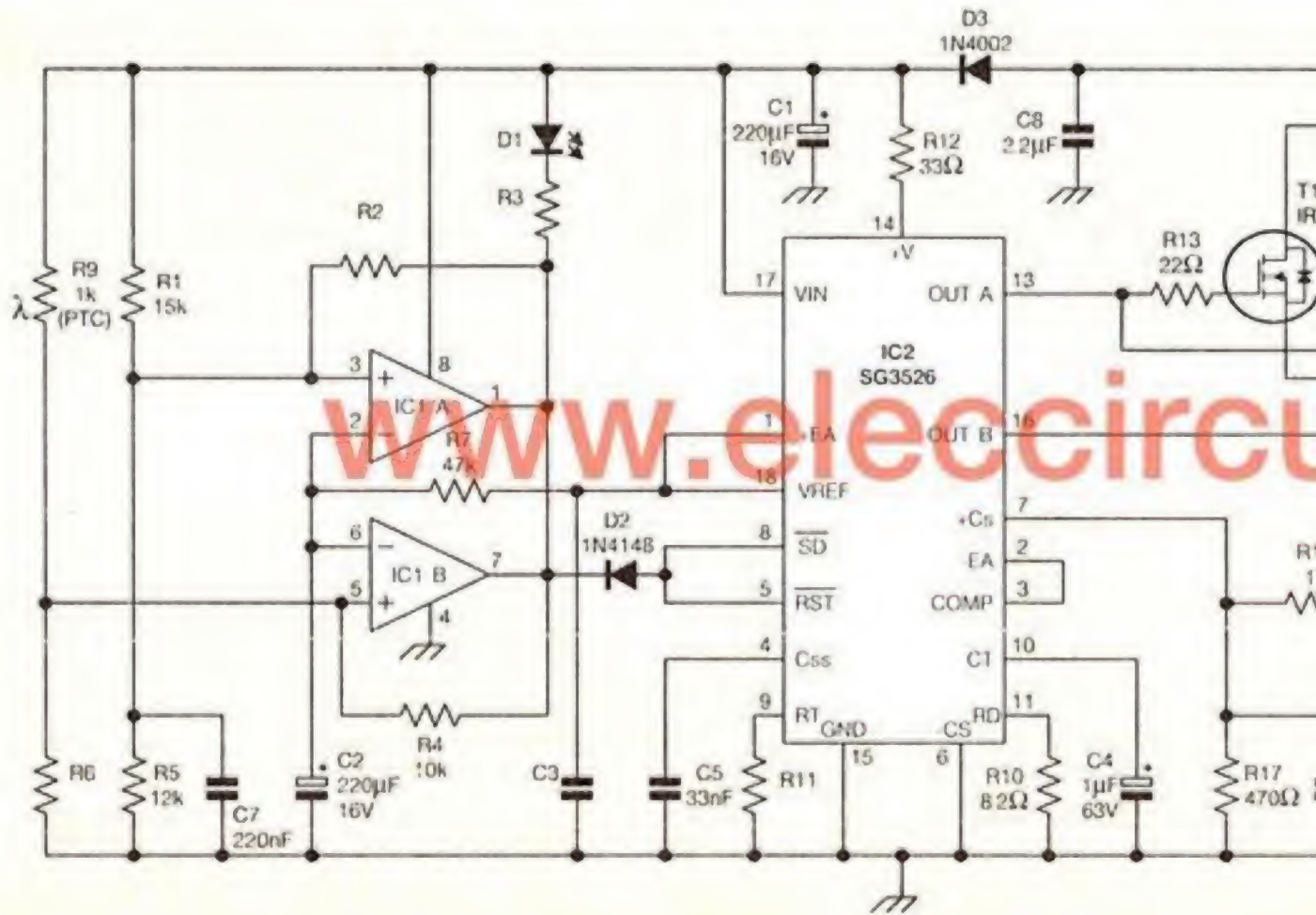

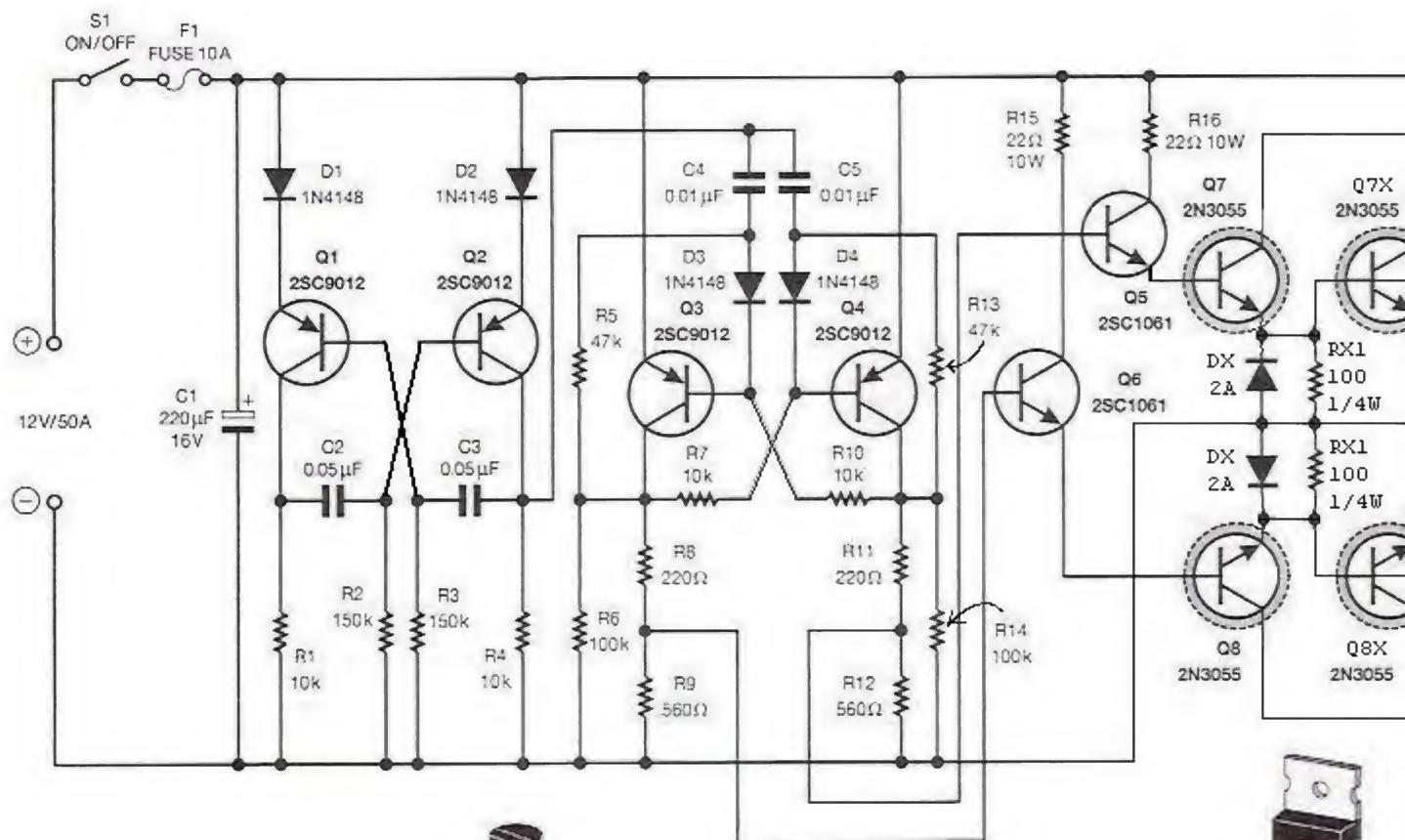




Q1-Q4




Q7,Q8

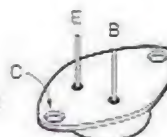


Q5,Q6



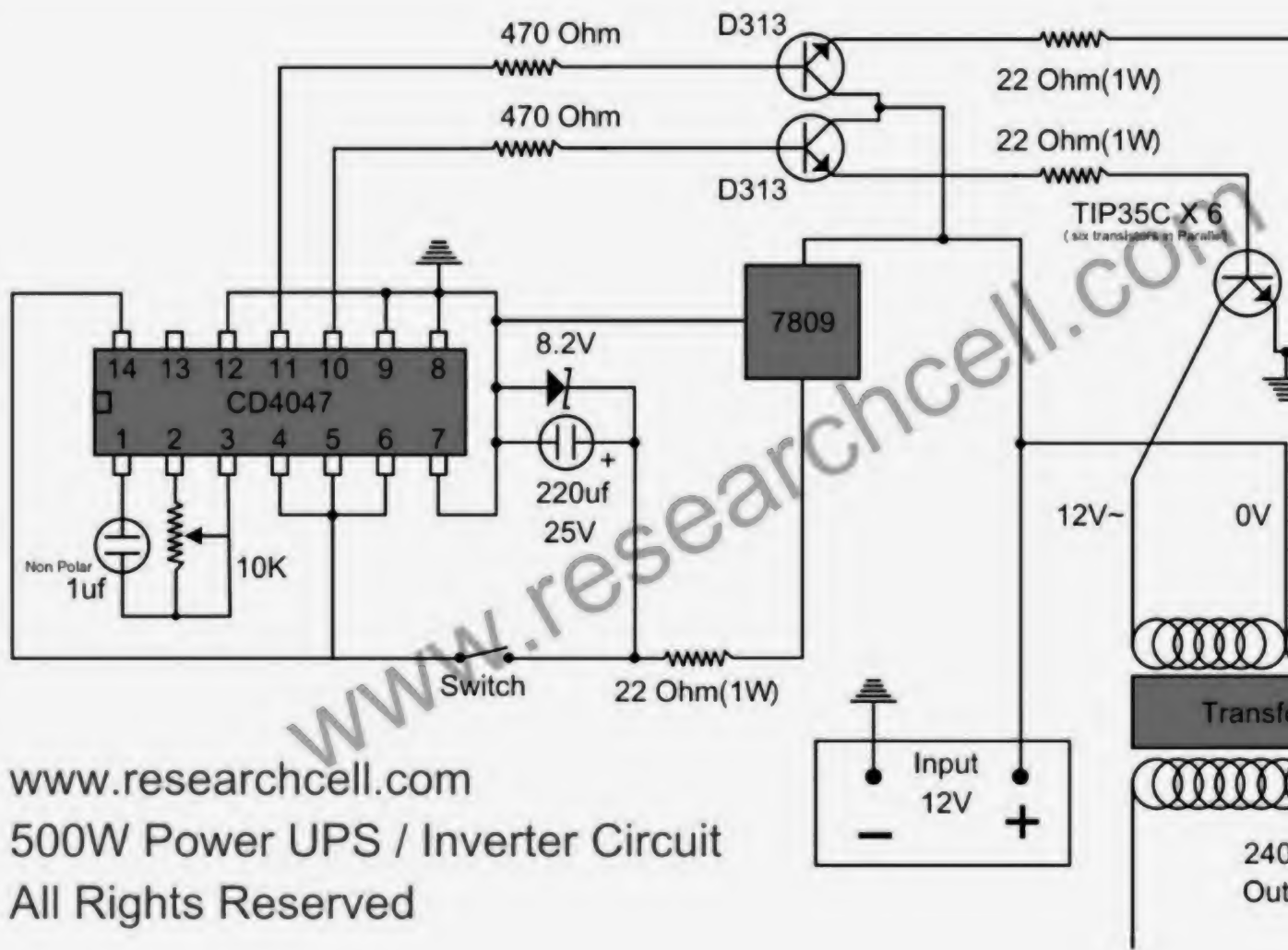




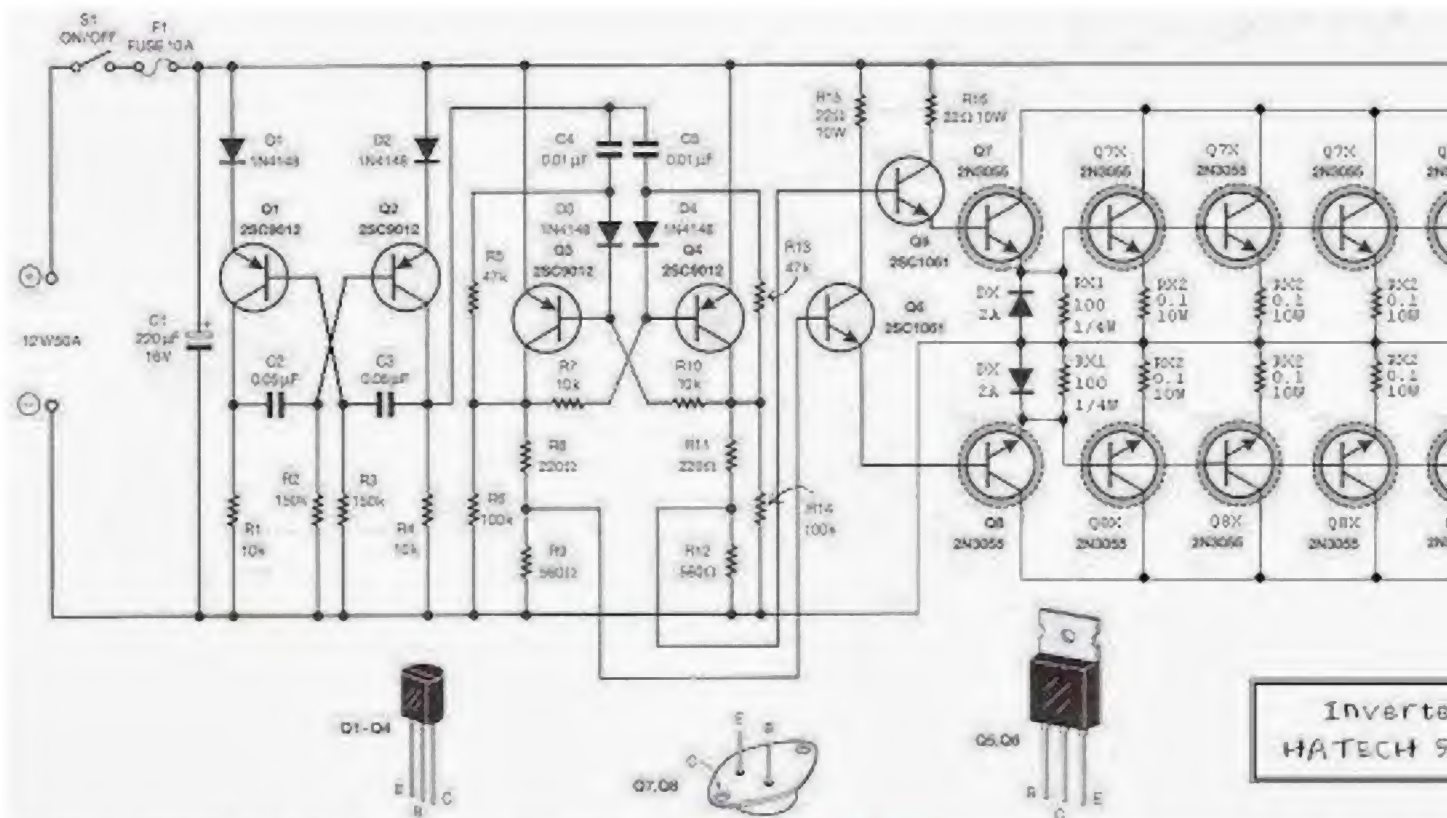

## Cheap 500W Inverter Circuit +12V DC

T1= 12-0-1

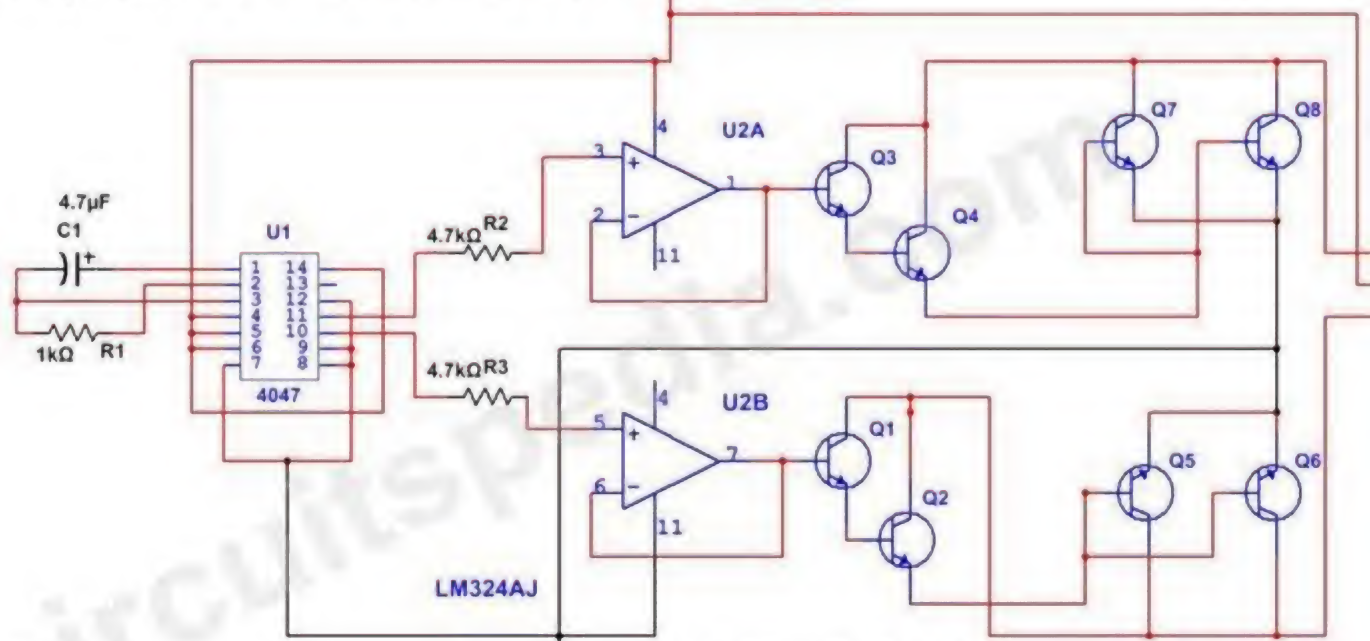

-Ve (12V DC)

U2A=U2B= LM324 (IC)

Q1,Q3 = C1061(Transistor)

Q2,Q4,Q5,Q6,Q7,Q8= 2N3055 (Power Transistor)